



CLASS : S.E. 5 E &TC

SUBJECT : DC

EXPT. NO. : 2

Roll No.: 22119

DATE:17th September, 2020

TITLE : STUDY OF DEMULTIPLEXER / DECODER.

PRE-REQUISITITES

FOR EXPT. : Definition of Demultiplexer/ Decoder, Implementation and operation of DEMUX/ Decoder using logic gates, Operation of Demultiplexer / Decoder IC-74LS138.(Refer Data-Sheet)

OBJECTIVE :

1. Verification of function table of IC-74LS138.
2. Design & Implement full adder circuit using IC-74LS138.
3. Design & Implement full subtractor circuit using IC-74LS138.
4. Design & Implement 3-bit Binary to Gray code converter-using IC-74LS138.
5. Design & Implement 3-bit Gray to Binary code converter-using IC-74LS138
6. Design & Implement following logical expression using IC-74LS138.

$$F1(A,B,C) = \sum_M(0,1,2,3)$$

$$F2(A,B,C) = \sum_M(2,3,4,5)$$

$$F3(A,B,C) = \sum_M(4,5,6,7)$$

APPARATUS :


Digital-Board, GP-4Patch-Cords, IC-74LS138, IC-74LS32, IC-74LS00 / IC-74LS04.

THEORY :

De-Multiplexer/Decoder is a combinational logic device, which has one input & many output, one output can be selected according to select input. IC-74LS138 is 3 to 8 Line Decoder/Demultiplexer. It is a 16-pin dual packaged IC, which has three enable pins (2-STROBE Active Low and one Active High). IC-74LS138 produces

Department of Electronics & Telecommunication Engineering

complementary output. i.e. the output of 74LS138 is Active Low. We can design any combinational circuits using IC-74LS138. DEMUX/Decoder performs reverse operation to that of Multiplexer.

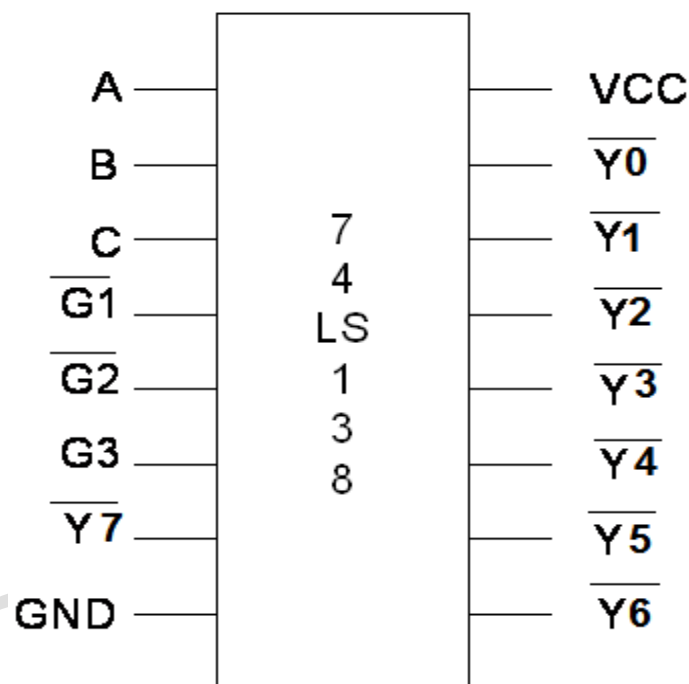
PIN Diagram :**PROCEDURE :**

1. Verify operation of IC 74138.
2. Design and implement 3 / 4 variables function using decoder and Verify its Truth Table.
3. Design and implement the logic diagram of Full adder / Subtractor circuit and Verify its Truth Table.
4. Design and implement 3-bit code converter circuit and Verify its Truth Table.

1) Verification of Function Table (IC-74LS138):

Select I/P						Active Low Output							
G1	G2	G3	A	B	C	\overline{Y}_0	\overline{Y}_1	\overline{Y}_2	\overline{Y}_3	\overline{Y}_4	\overline{Y}_5	\overline{Y}_6	\overline{Y}_7
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0

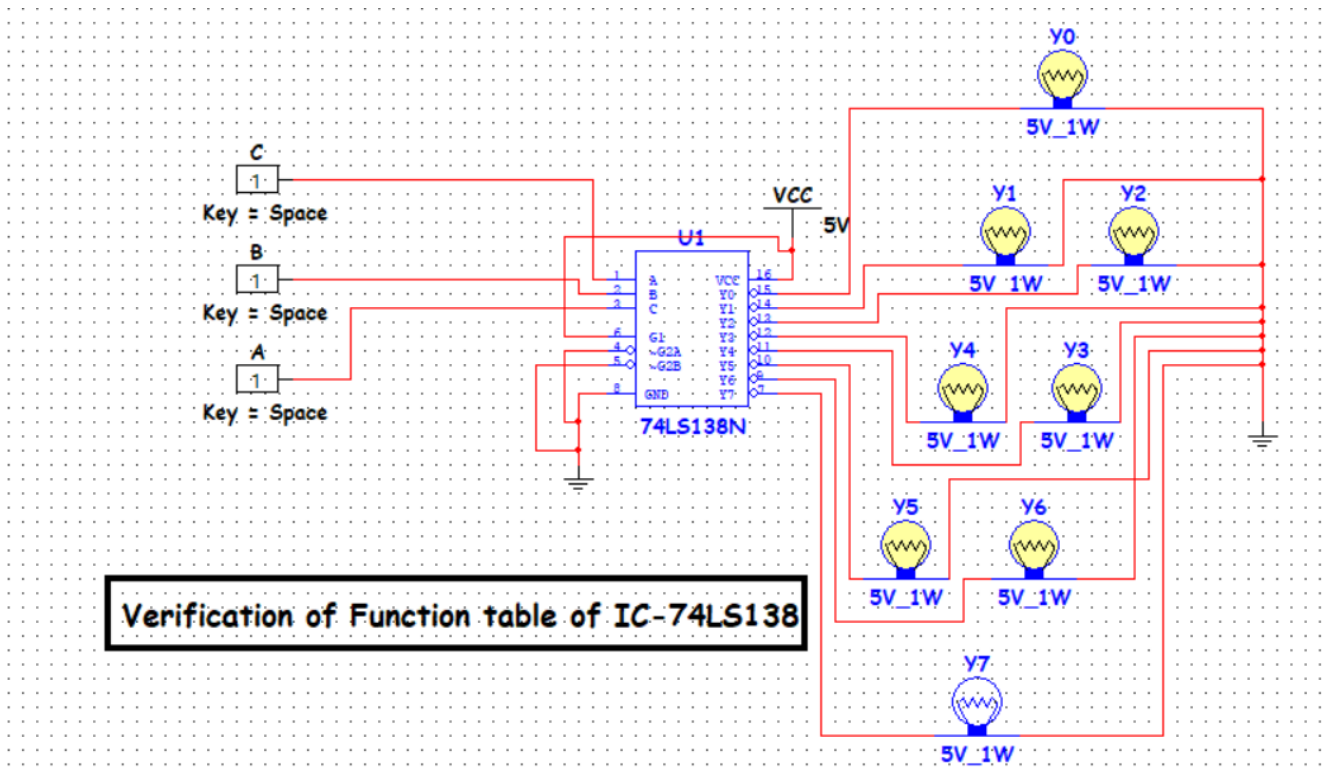Logic Diagram: (Verification of IC-74LS138)



2) Design of full adder using IC 74LS138


TRUTH -TABLE:

Select I/P			Output	
			Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \Sigma_m (1, 2, 4, 7)$$

$$\text{Carry} = \Sigma_m (3, 5, 6, 7)$$

Logic Diagram:

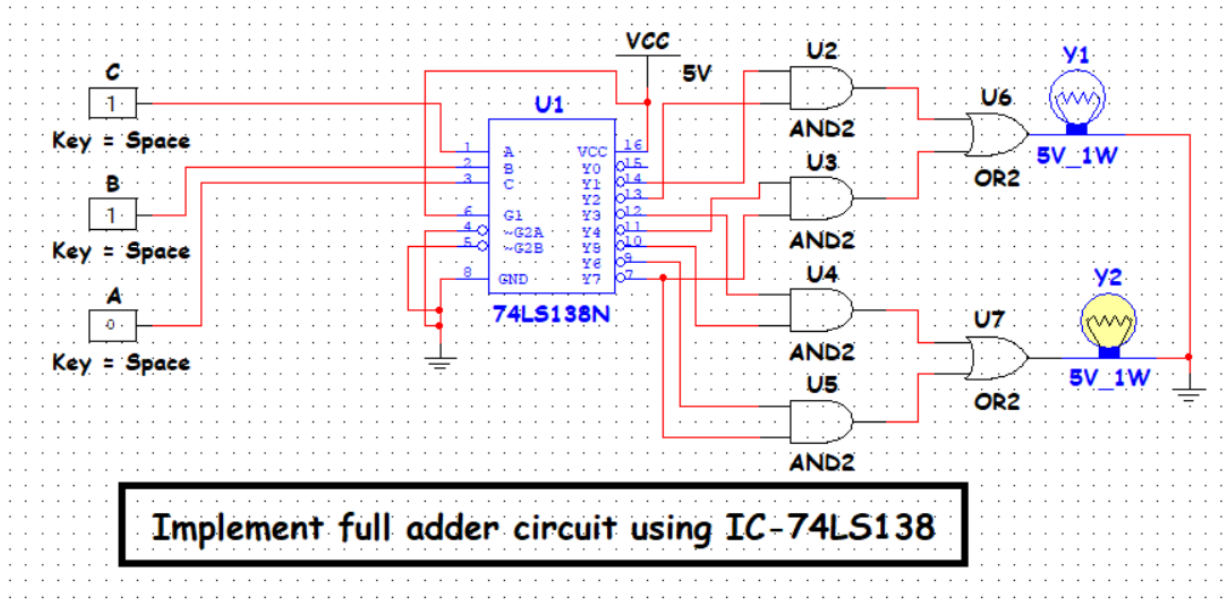


3) Full- Subtractor Circuit using IC74LS138

Select I/P			Output	
			DIFF	BORROW
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Difference} = \sum m(1, 2, 4, 7)$$

$$\text{Barrow} = \sum m(1, 2, 3, 7)$$

Logic Diagram:

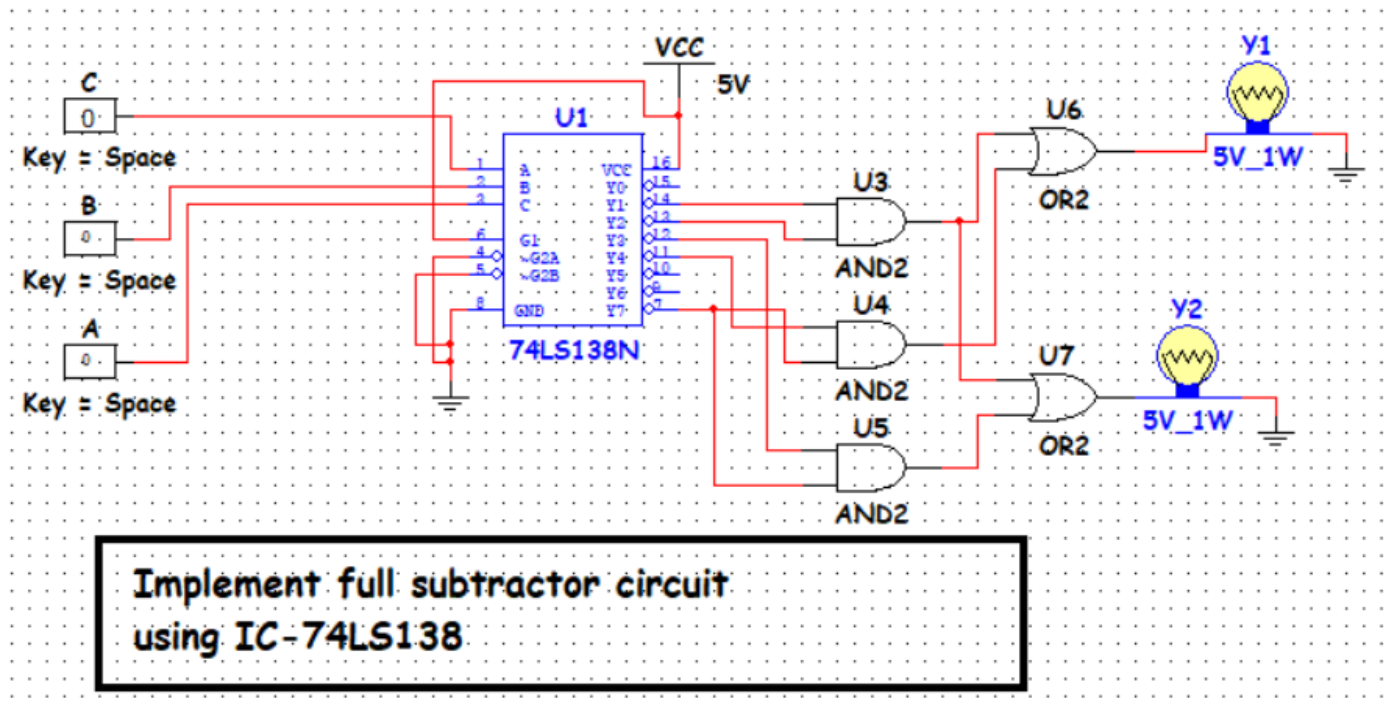


4) 3-bit Binary to 3-bit Gray code Converter:

Binary			Gray		
B2	B1	B0	G2	G1	G0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

$$=\Sigma m (4,5,6,7)$$

$$=\Sigma m (2,3,4,5)$$

$$=\Sigma m (1,2,5,6)$$

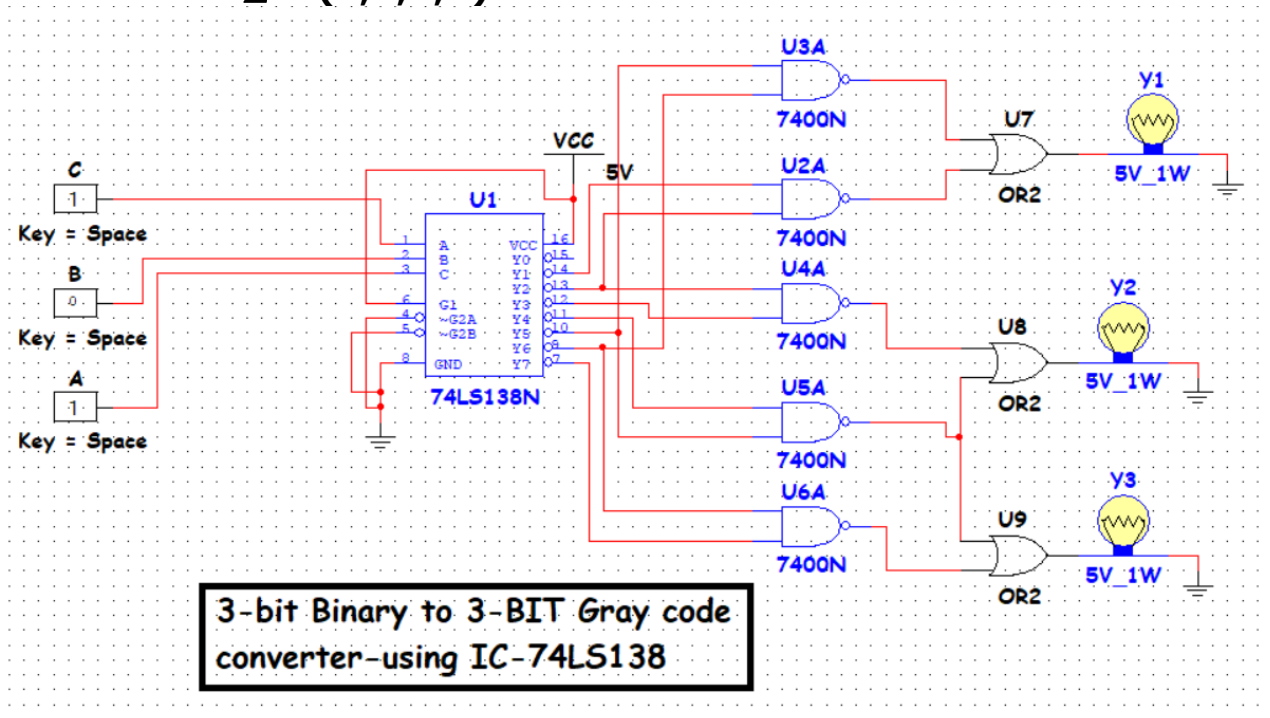


5) Logic Diagram: (3-bit Gray code To 3-bit Binary code Converter)

Gray			Binary		
G2	G1	G0	B2	B1	B0
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	1

$$=\Sigma m (4,5,6,7)$$

$$=\Sigma m (2,3,4,5)$$

$$=\Sigma m (1,2,4,7)$$

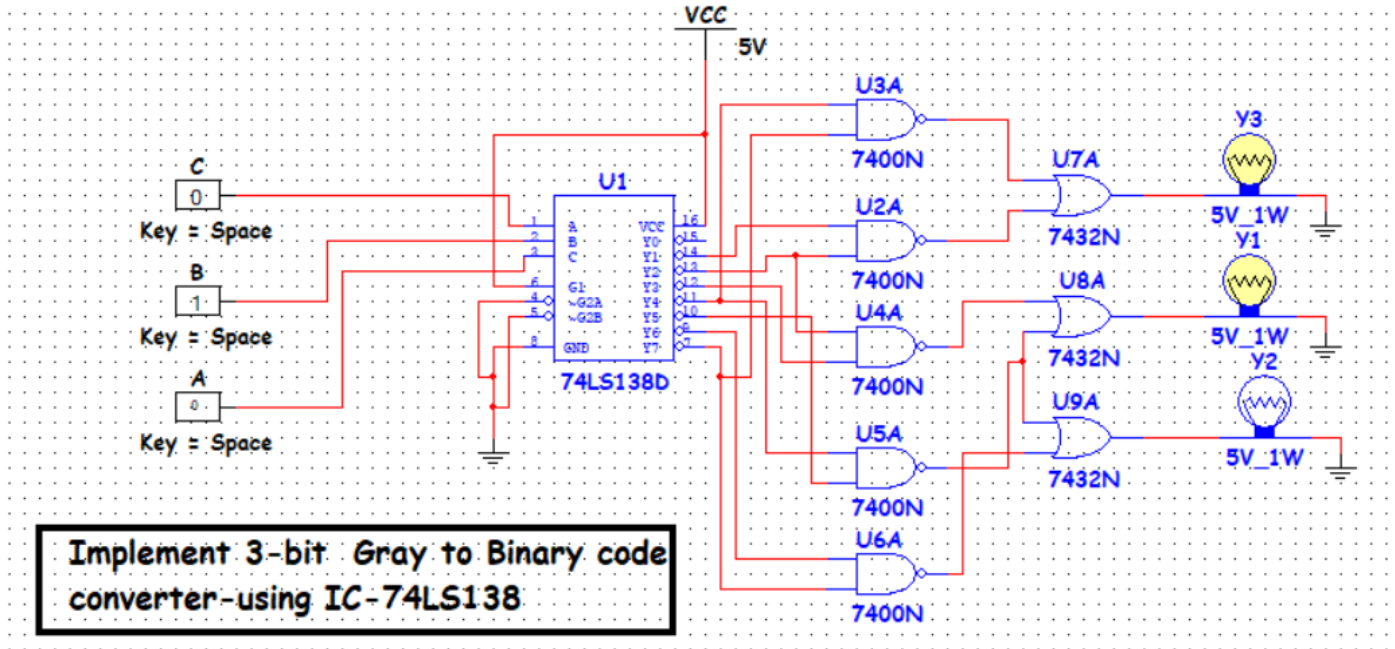

6).Design & Implement following logical expression using IC-74LS138.


$$F1 (A,B,C) = \sum_M (0,1,2,3)$$

$$F2 (A,B,C) = \sum_M (2,3,4,5)$$

$$F3 (A,B,C) = \sum_M (4,5,6,7)$$

Select I/P			Output		
A	B	C	F1	F2	F3
0	0	0	1	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	0	0	1

Logic Diagram:

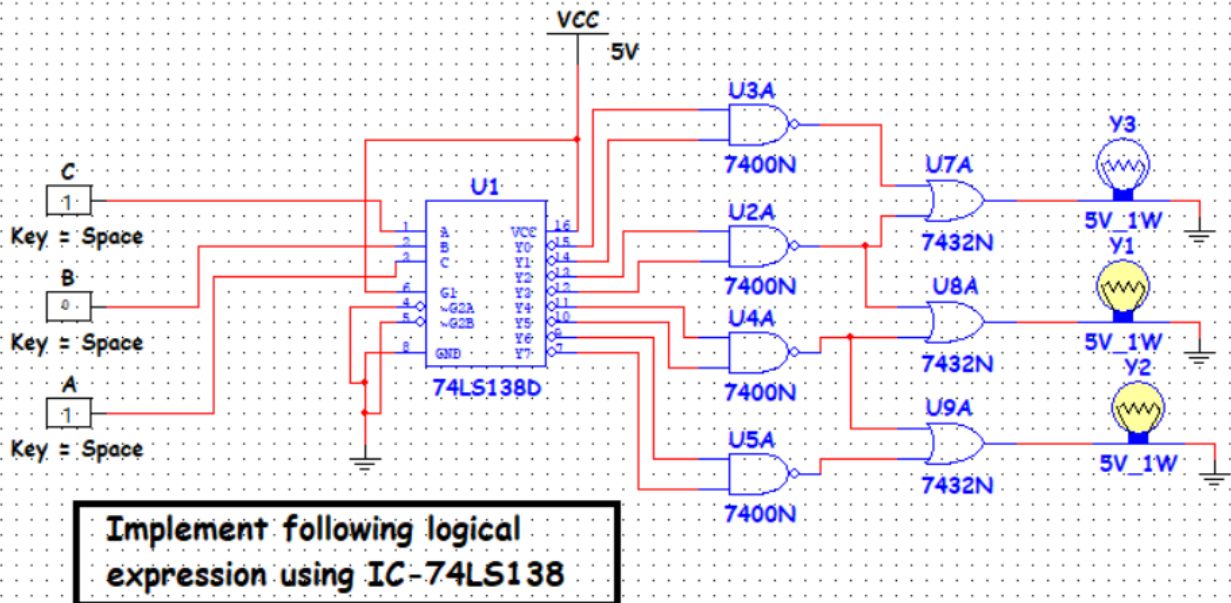

CONCLUSION :

- 1)Function table of IC74LS138 verified
- 2)succesfully designed and implemented full adder circuit with IC74LS138
- 3)succesfully designed and implemented full subtractor circuit with IC74LS138
- 4)Sucessfully designed and implemented 3bit binary to 3bit Gray code converter using IC74LS138
- 5) Sucessfully designed and implemented 3bit gray to 3bit binary Code converter
- 6)succesfully designed and implemented given logical expressions Using IC74LS138

REFERENCE:



- 1) : R.P. Jain , “Modern digital electronics” , 3rd edition
- 2) : A. Anand Kumar, “Fundamentals of digital circuits” 1st edition

Subject teacher Sign with Date

Remark