

Department of Electronics & Telecommunication

CLASS: S.E. E &TC SUBJECT: DC

EXPT. NO.: 6 DATE :05/12/2020

Roll No:22119

PRE-REQUISTITES FOR EXPT. :

Definition of Synchronous Counter

Implementation and operation of Synchronous Counter Using IC74LS90 or IC74LS93

OBJECTIVE:

- Design & Implement Mod-2 Counter using IC-74HC190
- Design & Implement Mod-5 Counter using IC-74HC190
- 3. Design & Implement Decade Counter using IC-74HC190
- 4. Design & Implement Mod-20 Counter using IC-74HC190
- 5. Design & Implement Mod-50 Counter using IC-74HC190
- 6. Design & Implement Mod-100 Counter using IC-74HC190

APPARATUS:

Digital-Board, Multisim

THEORY:


IC 74LS90 BCD counter.

Each of these monolithic counters contains four masterslave flip-flops and additional gating to provide a divide-bytwo counter and a three-stage binary counter for which the count cycle length is divide-by-five for the DM74LS90.

All of these counters have a gated zero reset and the DM74LS90 also has gated set-to-nine inputs for use in BCD nine's complement applications.

To use their maximum count length (decade or four bit binary), the B input is connected to the QA output. The input count pulses are applied to input A and the outputs are as described in the appropriate truth table. A symmetrical divide-by-ten count can be obtained from the DM74LS90 counters by connecting the QD output to the A input and applying the input count to the B input which gives a divide-by-ten square wave at output QA.

PIN DIAGRAM

 

IC 7490 Pin Diagram

Truth Table:

Count	Qd	Qc	Qb	Qa	_
(Start) 0	0	0	0	0	
1	0	0	0	1	
2	0	0	1	0	
3	0	0	1	1	_
4	0	1	0	0	_
5	0	1	0	1	_
6	0	1	1	0	
7	0	1	1	1	
8	1	0	0	0	IC 7490 Truth Tabl
9	1	0	0	1	
(New 10 Cycle)	0	0	0	0	

IC 74LS93 – 4 Bit Binary Counter

The SN54/74LS90, SN54/74LS92 and SN54/74LS93 are high-speed 4-bit ripple type counters partitioned into two sections. Each counter has a divide-by-two section and either a divide-by-five (LS90), divide-by-six (LS92) or divide-by-eight (LS93) section which are triggered by a HIGH-to-LOW transition on the clock inputs. Each section can be used separately or tied together (Q to CP) to form BCD, bi-quinary, modulo-12, or modulo-16 counters. All of the counters have a 2-input gated Master Reset (Clear), and the LS90 also has a 2-input gated Master Set (Preset 9).

PIN DIAGRAM

1	Сро		Cp1	14
2	MR1		NC	13
3	MR2	74	Q0	12
4	NC	7493	Q3	11
5	Vcc		GND	10
6	NC		Q1	9
7	NC		Q2	8


TRUTH Table:

LS93 TRUTH TABLE							
COLINIT	OUTPUT						
COUNT	Q ₀	Q ₁	Q ₂	Q ₃			
0	L	L	L	L			
1	н	L	L	L			
2	l L	Н	L	L			
3	н	Н	L	L I			
4	l L	L	Н	L			
5	н	L	Н	L			
6	l L	Н	Н	L			
7	н	Н	Н	L			
8	l L	L	L	н			
9	н	L	L	н			
10	l L	Н	L	н			
11	н	Н	L	н			
12	L	L	Н	н			
13	н	L	Н	н			
14	L	Н	Н	н			
15	н	Н	Н	н			


PROCEDURE :

- **1.** Make the connections as per the logic circuit of Mod-2 Counter, Mod-5 Counter, Mod-20 Counter, Mod-50 Counter, Mod-100 Counter
- 2.Make the connections as per the logic circuit of Decade Counter & Verify the truth table of IC7490.


Design & implement of Mod-2 counter

 


Design & implement of Mod-5 counter

 


Design & implement of Decade counter

 


Design & implement of Mod-20 counter

 

Design & implement of Mod-50 counter

 

Design & implement of Mod-100 counter

 

CONCLUSION:

- 1. We learnt pin configuration & Truth table of IC 74LS90 & IC74LS93.
- 2. We implement Mod-n counters.
- 3. We also verified the truth table of IC 74LS90

REFFRENCE:

- 1): R.P. Jain, "Modern digital electronics", 3rd edition
- 2): A. Anand Kumar, "Fundamentals of digital circuits" 1st edition

Subject teacher Sign with Date

Remark